



Final Presentation - P4 Accuracy of Approximate Circuits

FABIAN GARBER, SIMON HOWIND, KAGAN ÖZTEN,
MARTIN RESETARITS, PETER TRAUNMÜLLER

Table of Content

- Goals
- Methods
- Results
 - Error Analysis
 - Timing Analysis
 - Power Consumption & Area
- Conclusion

Goals


- Comparison of exact and approximate Full-Adder
- Power Consumption & Area evaluation
- Systematic error analysis
- VHDL implementation

Goals


- Comparison of exact and approximate Full-Adder
- Power Consumption & Area evaluation
- Systematic error analysis
- VHDL implementation

Methods

Methods – Design Comparison

 

Conventional Full Adder Circuit Design

 


Approximate Full Adder Circuit Design as proposed by Priyadharshni et al

Methods – Result Comparison

Input			Full Adder		INXA1		
x	y	C_{in}	C_{out}	s	C_{out}	s	
0	0	0	0	0	0	✓	0 ✓
0	0	1	0	1	1	✗	1 ✓
0	1	0	0	1	0	✓	1 ✓
0	1	1	1	0	1	✓	0 ✓
1	0	0	0	1	0	✓	1 ✓
1	0	1	1	0	1	✓	0 ✓
1	1	0	1	0	0	✗	0 ✓
1	1	1	1	1	1	✓	1 ✓


Methods - Error Analysis

 - For multi bit inputs, the error is not Hamming distance
- Error must be interpreted as number




Methods - Binary Decision Diagram

Input			Output
X[0]	X[1]	X[2]	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Methods – BDD Complexity

 


Example:


- 8 bit full adder
- $2^{(8*2)} = 65536$ input combinations
- BDDs for output bit „1“

<= Approximate: 31 nodes

Exact: 49 nodes =>

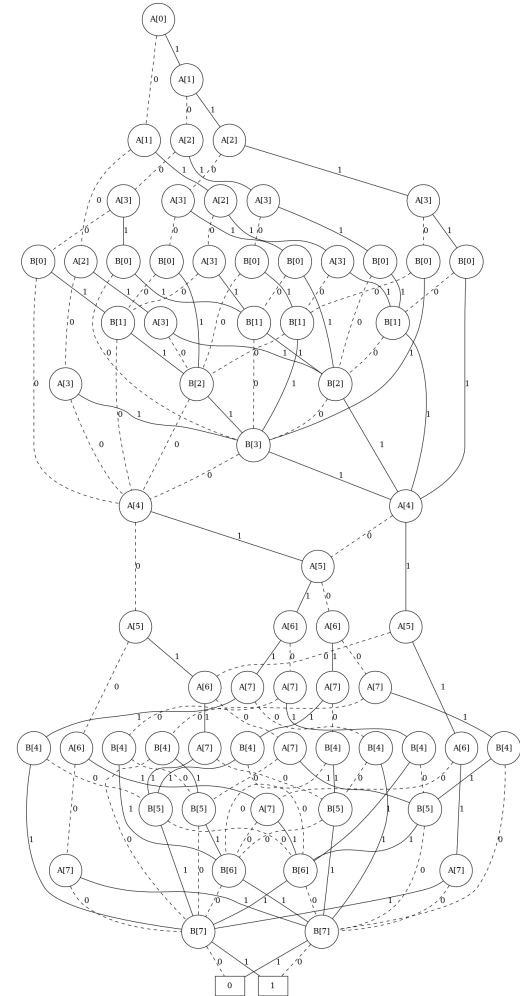

Methods – BDD Complexity

 

Example:


- 8 bit full adder
- $2^{(8*2)} = 65536$ input combinations
- BDDs for output bit „1“

<= Approximate: 31 nodes

Exact: 49 nodes =>

64 bit adder ?

$2^{(64*2)} = 3.4E38$ input combinations

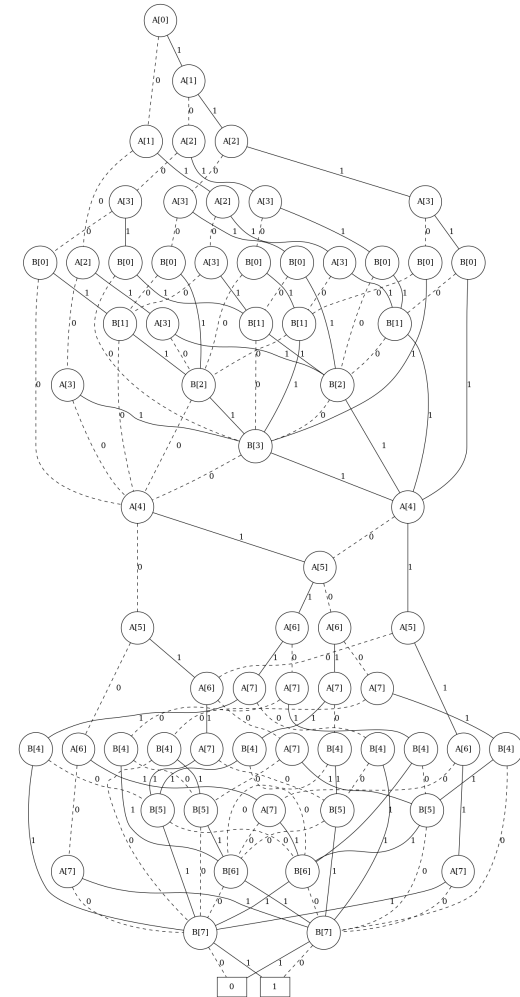


Methods - VHDL Implementation

- Vivado used for:
 - Power consumption analysis
 - Area analysis
 - Timing analysis


Methods - VHDL Implementation

- Exact vs. Approximate: reduced basic logic gate number

1-Bit Full Adder:

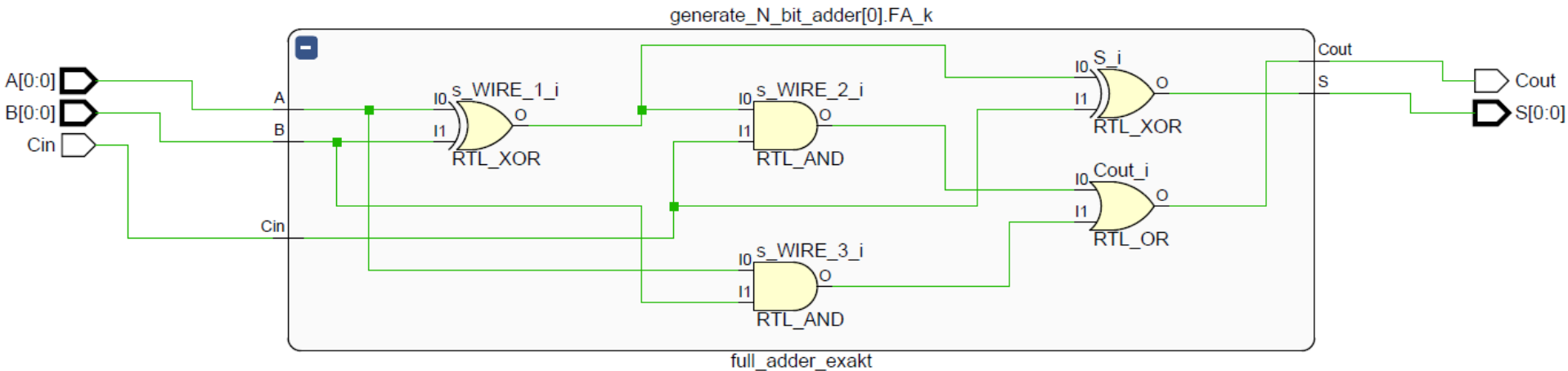


1-Bit Approximate Full Adder (INXA1):

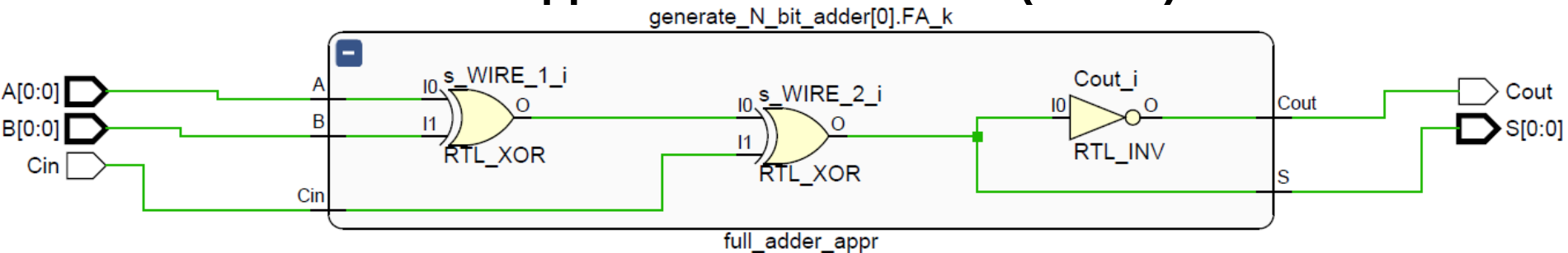

Results

Results - BDD: Error Analysis

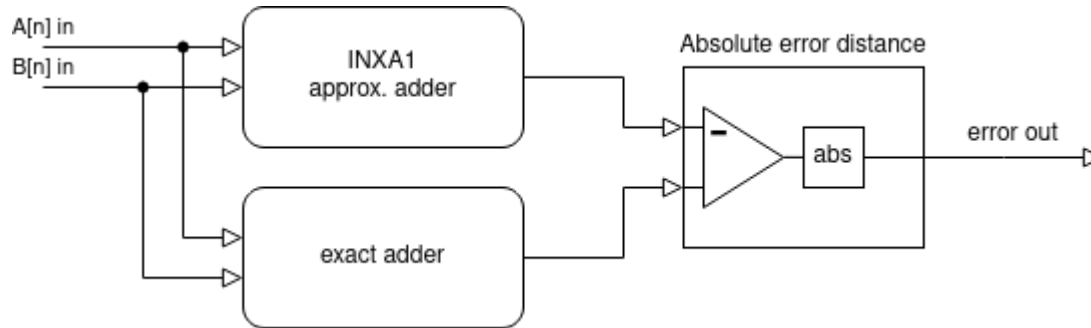


00	+	00	=	approx:	010	,	exact:	000	,	error out:	2
00	+	01	=	approx:	101	,	exact:	001	,	error out:	4
00	+	10	=	approx:	100	,	exact:	010	,	error out:	2
00	+	11	=	approx:	011	,	exact:	011	,	error out:	0
01	+	00	=	approx:	101	,	exact:	001	,	error out:	4
01	+	01	=	approx:	010	,	exact:	010	,	error out:	0
01	+	10	=	approx:	011	,	exact:	011	,	error out:	0


...

Results - BDD: Error

- Error BDD for 8 bit adders

 

Results – Visual Error Analysis

 

Results – Timing Analysis

Type	A	B	C	S	C _{out}
4 Bit Exact	2,5	2,5	2,5	6,235	3,814
4 Bit Approx.	2,5	2,5	2,5	7,830	9,24
16 Bit Exact	2,5	2,5	2,5	6,460	3,847
16 Bit Approx.	2,5	2,5	2,5	9,39	9,999





Timing Analysis – Signal Rate in Mega transactions (Mtr) per second

Results - Power Consumption

EXACT

APPROXIMATE

4 BIT

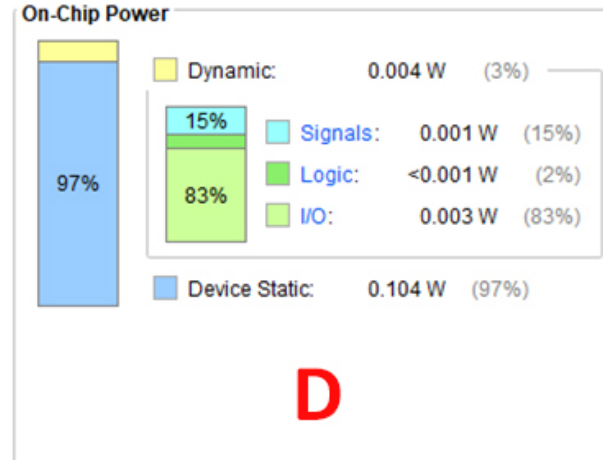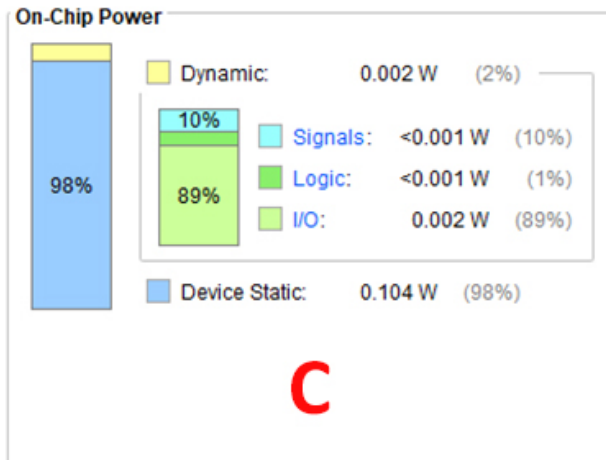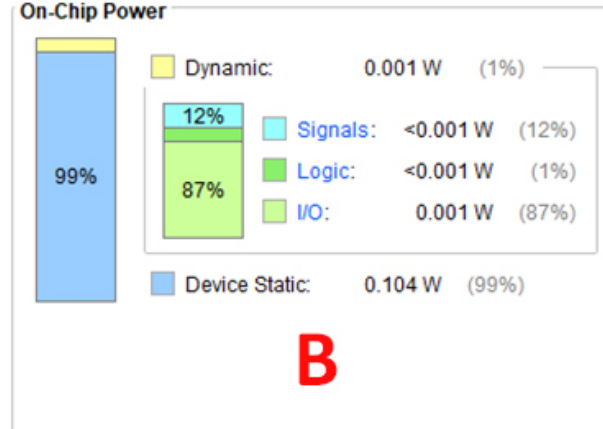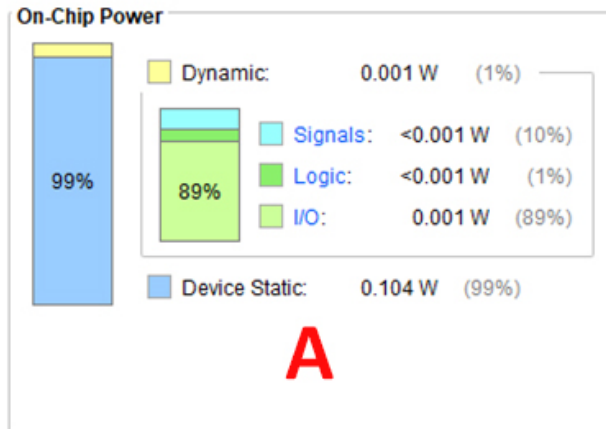

16 BIT

Results - Area Analysis

Used metric for area: Gate Count in adders

TYPE	XOR	OR	AND	NOT	Basic Gates in Total
1 Bit Exact	2	1	2	X	11
4 Bit Exact	8	4	8	X	44
8 Bit Exact	16	8	16	X	88
16 Bit Exact	32	16	32	X	176
1 Bit Appro.	2	X	X	1	9 (-3)
4 Bit Appro.	8	X	X	4	36 (-8)
8 Bit Appro.	16	X	X	8	72 (-16)
16 Bit Appro.	32	X	X	16	144 (-32)

= ~18.2% less

XOR = 2 AND + 1 OR + 1 NOT = 4 Basic Gates

Conclusion

Achieved Goals

- ✓ Comparison of exact and approximate Full-Adder
- ✓ Power Consumption & Area evaluation
- ✓ Systematic error analysis
- ✓ VHDL implementation

Outlook

- Implementation on FPGA board
- Using an actual design

